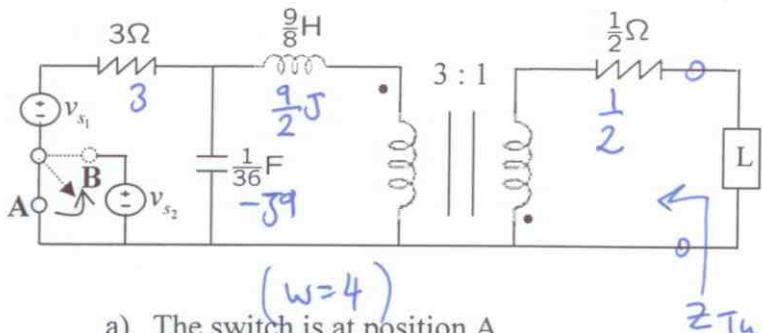


Question 1 (18 pts)



$$v_{s_1}(t) = A \cos(4t) \text{ V},$$

$$v_{s_2}(t) = A \cos(4t + 60^\circ) \text{ V}$$

- a) The switch is at position A.

The load is adjusted for the maximum power transfer.

The real power delivered to the load is 300 Watts.

Find the reactive power delivered to the load.

- b) The switch is moved to position B.

Find the real power delivered to the load.

$$a) Z_L = Z_{T_h}^* ; \quad Z_{T_h} = \left[ (3 \parallel -j9) + \frac{9}{2}j \right] \frac{1}{9} + \frac{1}{2}$$

$$= \left[ \left( \frac{1}{3} \parallel -j \right) + \frac{j}{2} \right] + \frac{1}{2}$$

$$= \left[ \frac{-j/3}{\frac{1}{3} - j} + \frac{j}{2} \right] + \frac{1}{2}$$


$$= \left[ -j \frac{(1+3j)}{10} + \frac{j}{2} \right] + \frac{1}{2}$$

$$= 0.8 + j 0.4$$


$$Z_L = 0.8 - j 0.4 \rightarrow P_{\text{Load}} = (I_{\text{Load}}^{\text{RMS}})^2 \cdot (0.8) = 300 \text{ Watt}$$

$$Q_{\text{Load}} = (I_{\text{Load}}^{\text{RMS}})^2 \cdot (-0.4) = -150 \text{ Var.}$$

given

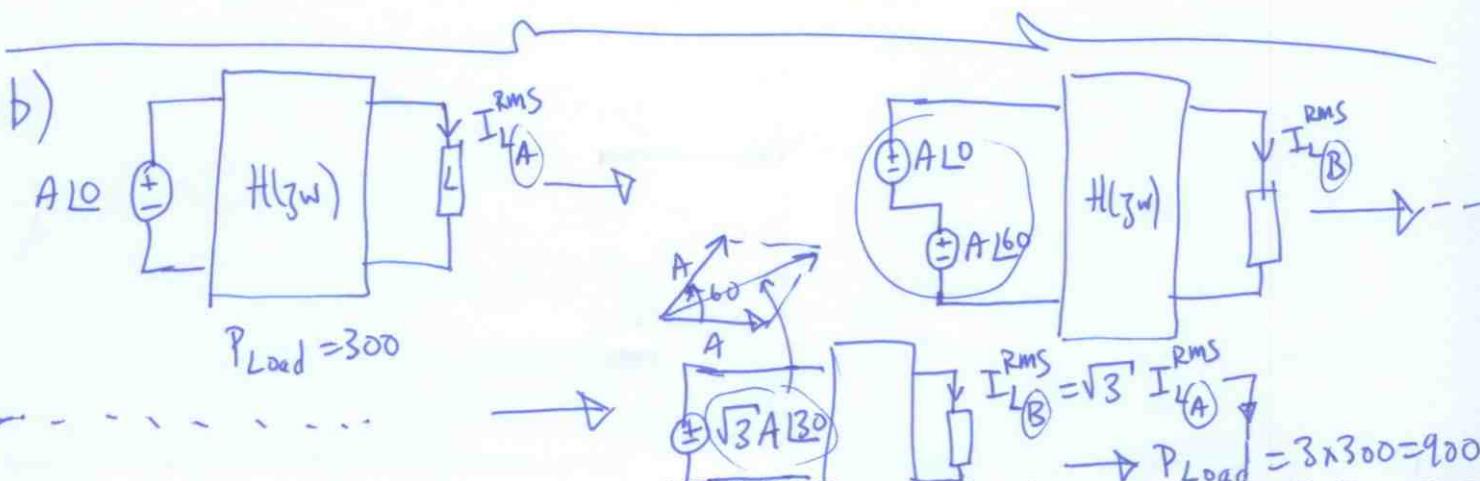

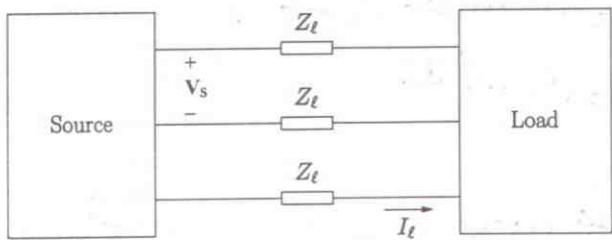Question 2 (24 pts) Consider the following balanced three-phase circuit with  $\Delta$ -connected inductive load.



$$P_{\text{Load}} = 14.4 \text{ kW},$$

$$Z_t = \frac{1}{3} + j \frac{4}{9} \Omega,$$

The percent efficiency,  $\eta = 90\%$ ,

$$V_{S,\text{eff}} = \frac{2000}{3\sqrt{3}} \text{ V}_{\text{rms}},$$


Find:

- +6 a) the effective value of the line current  $I_L$ ,
- +6 b) the total complex power supplied by the source,
- +6 c) the effective value of the line-to-line voltage at the load side,
- +6 d) the per phase impedance of the load.

$$a) \frac{P_{\text{Load}}}{P_{\text{Sup}}} = 0.9 \rightarrow P_{\text{Sup}} = \frac{14.4 \text{ kW}}{0.9} = 16 \text{ kW} \rightarrow P_{\text{Line Loss}} = 1.6 \text{ kW}$$

$$\rightarrow P_{\text{Line Loss}} = 1600 = 3(I_L)^2 / 3 \rightarrow I_L^{\text{RMS}} = 40 \text{ A RMS}$$

$$b) |S_{\text{Sup}}| = \sqrt{3} V_S I_L^{\text{RMS}} = \sqrt{3} \frac{2000}{3\sqrt{3}} \cdot 40 = \frac{80}{3} \text{ kVA}$$

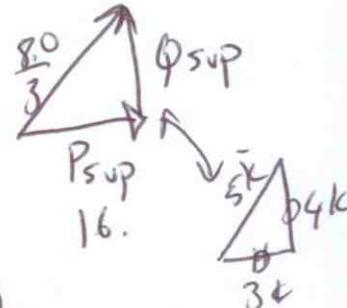

$$Q_{\text{Sup}} = \frac{64}{3} \text{ kVAR.} \quad | \quad S_{\text{Sup}} = 16 + j \frac{64}{3} \text{ kVA} \quad (b)$$

$$c) S_{\text{Load}} = S_{\text{Sup}} - S_{\text{Line}} = \left( 16 + j \frac{64}{3} \right) - \left( 1.6 + j (1.6) \frac{4}{3} \right) \\ = 0.9 \left( 1.6 + j \frac{64}{3} \right) \text{ kVA.}$$


$$|S_{\text{Load}}| = \sqrt{3} (I_L^{\text{RMS}}) (V_{\text{Line, RMS}}^{\text{Load}}) \rightarrow (0.9) \frac{80000}{3} = \sqrt{3} \cdot 40 \cdot V_{\text{Line, RMS}}^{\text{Load}}$$

$$d) S_{\text{Load}, \phi} = 0.3 \left( 16 + j \frac{64}{3} \right)^{\frac{3}{2}} = 40^2 \text{ VA}$$

$$\rightarrow Z_Y = 3 + j 4 \rightarrow Z_D = 3 Z_Y = 9 + j 12 \Omega$$

$$V_{\text{Line}}^{\text{Load}} = (2000) 0.9 = \frac{600}{\sqrt{3}} = 200 \sqrt{3} \text{ V}$$

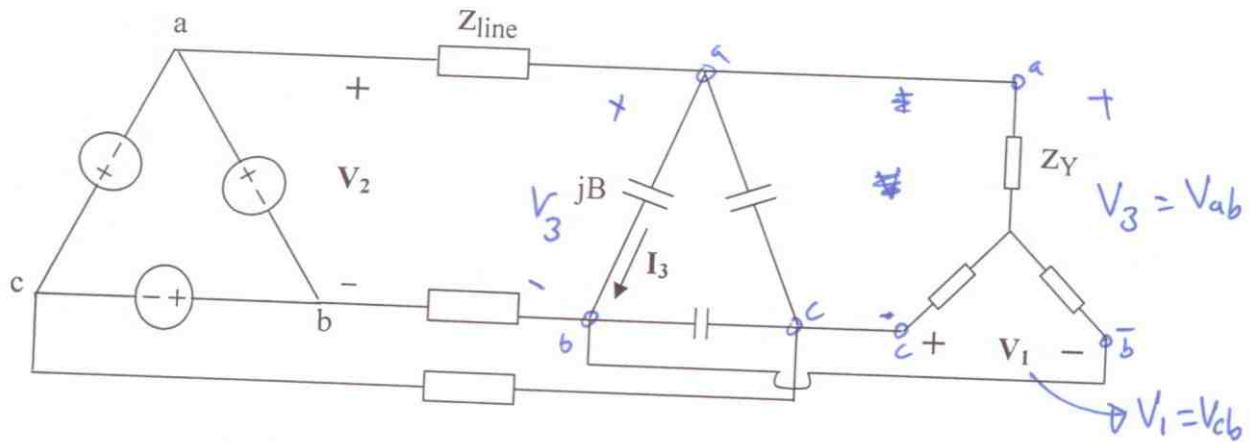Question 3 (24 pts) Given a balanced 3-phase circuit with a positive phase sequence.



$$f = 50 \text{ Hz}, \quad Z_{\text{line}} = 0.4 + j1.2 \Omega, \quad Y_Y = \frac{2}{9} - j\frac{1}{6} \text{ mhos}$$

$$V_1 = 180\sqrt{15} \angle 120^\circ \text{ V}_{\text{rms}}$$

The power factor of the Y load – capacitor bank combination is  $\frac{2}{\sqrt{5}}$  lagging.

a) (12 pts) Find

- i) the complex power delivered to the Y-load,
- ii) the per phase capacitance of the capacitor bank,
- iii) the complex power supplied by the source,
- iv) the percent efficiency.

b) (12 pts) Find  $i_3(t)$  and  $v_2(t)$ .

$$\begin{aligned} \text{i) } S_{\text{load}} &= 3 \frac{V_1^2}{Z_Y} = 3 \left( \frac{180\sqrt{15}}{\sqrt{3}} \right)^2 \left( \frac{2}{9} + j\frac{1}{6} \right) \\ &= 180.15 (40 + j30) \\ &= 27000 (4 + j3) \end{aligned}$$

$$\text{ii) } S_{\text{combi}} = 27000 (4 + j4.5)$$

$$S_{\text{cap}} = -j27000$$

$$S_{\text{cap}\phi} = -j9000 = \frac{|V_1|^2}{Z_{\text{cap}}}$$

$$Z_{\text{cap}} = \frac{180^2 \cdot 15}{9000} (-j) = -j54$$

$$C = \frac{1}{2\pi 54} \approx \frac{1}{3(5400)} = 60 \mu\text{F}$$

$$\text{iii) } S_{\text{combi}} = \sqrt{3} \vartheta_{\text{line}}^{\text{combi}} I_{\text{line}}$$

$$|(27000)(4 + j3)| = \sqrt{3} 180\sqrt{15} \cdot I_{\text{line}}$$


$$\frac{(27000)^2}{2\sqrt{3}} \cdot \frac{1}{\sqrt{3}} \cdot \frac{1}{180\sqrt{15}} = I_{\text{line}}$$

$$I_{\text{line}} = 100 \text{ A (rms)}$$

$$S_{\text{line}} = 3 I_{\text{line}}^2 (0.4 + j1.2) = 12 + j36 \text{ kVA}$$

$$\begin{aligned} \text{iv) } S_{\text{sup}} &= (27 \times 4 + j27 \times 2) \\ &\quad (12 + j36) \text{ kVA} \\ &= 120 + j90 \text{ kVA} \end{aligned}$$

$$\eta = \frac{(27)(4)}{120} = 90\%$$

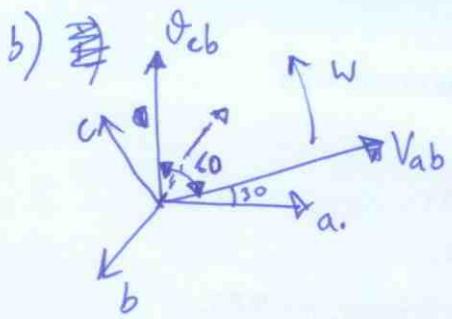

$$V_{ab} = V_{cb} \angle -60^\circ$$

$$V_{ab} = (190\sqrt{15} \angle 120^\circ) (\angle -60^\circ)$$


$$= 190\sqrt{15} \angle 60^\circ$$

$$i_3 = \frac{\sqrt{3}}{-j\beta} = \frac{180\sqrt{15} \angle 60^\circ}{-j54} = \frac{10\sqrt{5}}{\sqrt{3}} \angle 150^\circ \rightarrow i_3(t) = 10\sqrt{\frac{5}{3}} \cos(2\pi 50t + 150^\circ)$$

$A_{RMS}$

---

V<sub>2</sub>(t)

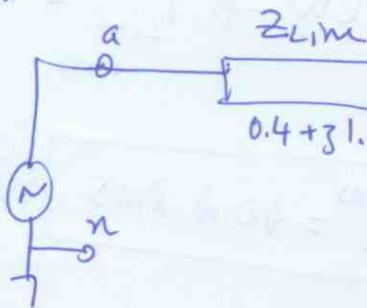

$$V_{an} = V_{a'b} \angle -30^\circ$$

$$= 190\sqrt{15} \angle 30^\circ$$

$$Z_{Tot} = Z_T \parallel \left( \frac{-j\beta}{\frac{3}{3}} \right)^{-1}$$

$$= \left[ \left( \frac{2}{9} - j\frac{1}{6} \right) + \left( +j\frac{1}{18} \right) \right]^{-1}$$

$$= \left( \frac{2}{9} (1-j) \right)^{-1} = \frac{9}{2} \left( \frac{1+j}{2} \right)$$

$$V_{an} = \left( \frac{190\sqrt{15} \angle 30^\circ}{\frac{9}{4}\sqrt{2} \angle 45^\circ} \right) \left( \frac{9}{4} + j\frac{9}{4} + 0.4 + j1.2 \right)$$

$$V_{an} = 80\sqrt{\frac{15}{2}} \angle -15^\circ (2.65 + j3.45)$$

$$V_2 = V_{an} \sqrt{3} \angle +30^\circ = 240\sqrt{\frac{5}{2}} \angle 15^\circ (2.65 + j3.45)$$

$$V_2(t) = |V_2| \cos(2\pi 50t + \delta V_2) V_0 \text{ RMS}$$

Question 4 (10 pts)

In a balanced three-phase load with a positive phase sequence, the complex power is:

$$S = 1500 + j500\sqrt{3} \text{ VA}$$




What are the wattmeter readings?

**NOTE:** You have to show your derivations to obtain credit for this question.

$$WM_1 \Rightarrow Re \left\{ V_{ab} I_a^* \right\}$$


$$WM_2 \Rightarrow Re \left\{ V_{ac} I_a^* \right\}$$

$$\begin{aligned} WM_1 &\Rightarrow Re \left\{ \sqrt{3} V_{ph}^{RMS} [130] I_{ph}^{RMS} [1 + \theta_L] \right\} \\ &= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \cos(30 + \theta_L) \\ &= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} [\cos 30 \cos \theta_L - \sin 30 \sin \theta_L] \\ &= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \frac{\sqrt{3}}{2} \cos \theta_L - \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \frac{1}{2} \sin \theta_L \\ &= \frac{\sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \cos \theta_L}{2} - \frac{3 V_{ph}^{RMS} I_{ph}^{RMS} \sin \theta_L}{\sqrt{3} \cdot 2} \\ &= \frac{1500}{2} - \frac{500\sqrt{3}}{\sqrt{3} \cdot 2} \\ &= 500 \text{ Watt.} \end{aligned}$$

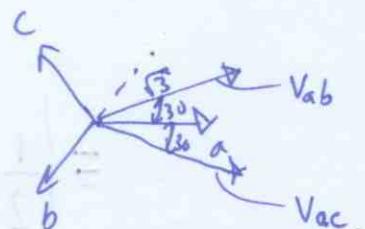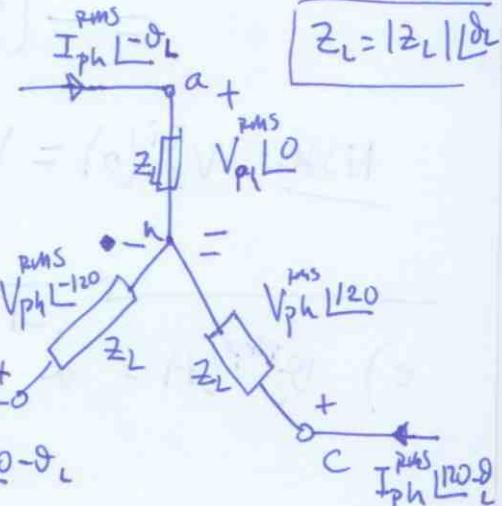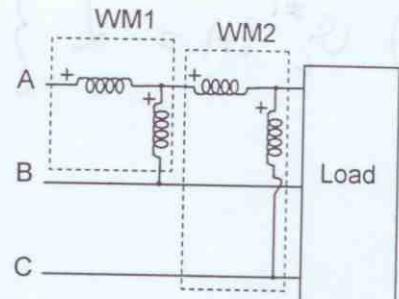

$$\begin{aligned} WM_2 &\Rightarrow Re \left\{ \sqrt{3} V_{ph}^{RMS} [130] I_{ph}^{RMS} [1 - \theta_L] \right\} \\ &= \sqrt{3} V_{ph}^{RMS} I_{ph}^{RMS} \cos(-30 + \theta_L) \\ &= \frac{1500}{2} + \frac{500\sqrt{3}}{\sqrt{3} \cdot 2} = 1000 \text{ Watt.} \end{aligned}$$

Question 5 (24 pts)

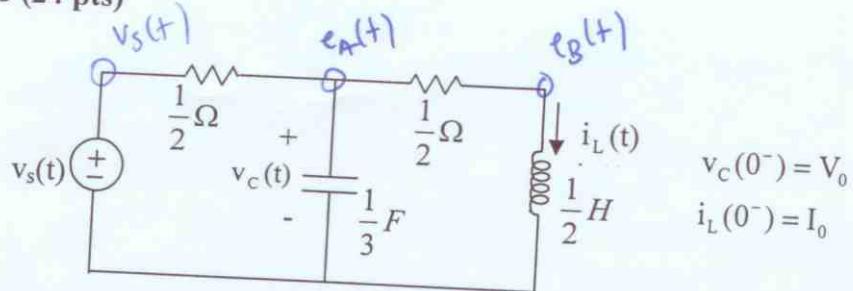


$$v_C(0^-) = V_0$$

$$i_L(0^-) = I_0$$

- +4 a) Obtain the node equations in time domain, and put them in matrix form.
- +4 b) Transform the node equation in part (a) to the s-domain.
- +4 c) Transform the circuit to the s-domain, and then obtain the node equations in matrix form.
- +4 d) Express  $V_C(s)$  in terms of  $V_s(s)$  and  $V_0$  and  $I_0$ .
- +4 e) Find the zero-input response for  $v_C(t)$ .
- +4 f) Find the unit step response for  $v_C(t)$ .

$$\left. \begin{array}{l} \text{a) KCL at } e_A \rightarrow (e_A - v_s)2 + \frac{1}{3} \dot{e}_A + (e_A - e_B)2 = 0 \\ \text{KCL at } e_B \rightarrow (e_B - e_A)2 + I_0 + 2\bar{D}\{e_B\} = 0 \end{array} \right\} \begin{bmatrix} 4 + \frac{1}{3} & -2 \\ -2 & 2 + 2\bar{D} \end{bmatrix} \begin{bmatrix} e_A \\ e_B \end{bmatrix} = \begin{bmatrix} 2v_s \\ -I_0 \end{bmatrix}$$
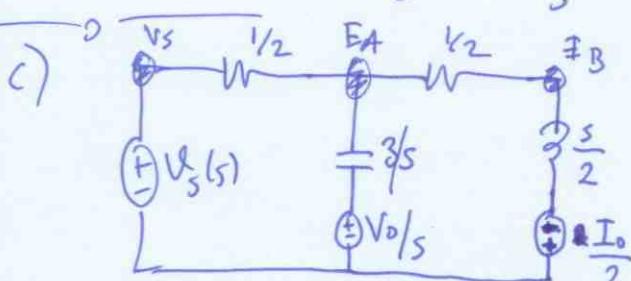
$$\left. \begin{array}{l} \text{b) } (E_A - V_s)2 + \frac{1}{3}(sE_A - V_0) + (E_A - E_B)2 = 0 \\ (E_B - E_A)2 + \frac{I_0}{s} + 2\frac{E_B}{s} = 0 \end{array} \right\} \begin{bmatrix} 4 + \frac{s}{3} & -2 \\ -2 & 2 + \frac{2}{s} \end{bmatrix} \begin{bmatrix} E_A(s) \\ E_B(s) \end{bmatrix} = \begin{bmatrix} 2V_s(s) \\ \frac{V_0}{s} - I_0 \end{bmatrix}$$



$$\begin{bmatrix} 2 + 2 + \frac{s}{3} & -2 \\ -2 & 2 + \frac{2}{s} \end{bmatrix} \begin{bmatrix} E_A(s) \\ E_B(s) \end{bmatrix} = \begin{bmatrix} \frac{V_0}{3} + 2V_s(s) \\ -I_0/s \end{bmatrix}$$

$$\text{d) } V_c(s) = E_A(s) \rightarrow E_A(s) = \frac{1}{\Delta} \left[ 2 + \frac{2}{s} \mid \text{det} + 2 \right] \begin{bmatrix} \frac{V_0}{3} + 2V_s(s) \\ -I_0/s \end{bmatrix}$$

$$\Delta = \left( 4 + \frac{s}{3} \right) \left( 1 + \frac{1}{s} \right) \cdot 2 - 4$$

$$= \frac{2s}{3} + \frac{14}{3} + \frac{8}{s} = \frac{2}{3s} (s^2 + 7s + 12) = \frac{2}{3s} (s+4)(s+3)$$

$$E_A(s) = \left[ 1 + \frac{1}{s} \mid \cancel{\frac{s}{s}} \right] \begin{bmatrix} \frac{V_0}{3} + 6V_s(s) \\ -3I_0/s \end{bmatrix} \cdot \frac{s}{\cancel{s}(s+4)(s+3)}$$

$$= \frac{(s+1)(V_0 + 6V_s(s)) - 3I_0}{s(s+4)(s+3)} = \frac{(s+1)6V_s(s)}{s(s+4)(s+3)} + \frac{(s+1)V_0 - 3I_0}{s(s+4)(s+3)}$$

$$d) V_C^{zi}(t) = \mathcal{L}^{-1} \left\{ \frac{(s+1)V_0 - 3I_0}{(s+4)(s+3)} \right\}$$

$$\rightarrow \frac{-2V_0 - 3I_0}{s+3} + \frac{3V_0 + 3I_0}{s+4}$$

$$= -(2V_0 + 3I_0)e^{-3t} + 3(V_0 + I_0)e^{-4t} \quad V. \quad t > 0$$

Note:  $V_C^{zi}(0) = V_0$  as expected. (Also  $\lim_{s \rightarrow \infty} V_C^{zi}(s) = V_0$ )

$$e) V_C^{step}(t) = \mathcal{L}^{-1} \left\{ \frac{6(s+1)/s}{(s+4)(s+3)} \right\}$$

$$\rightarrow \frac{Y_2}{s} + \frac{-4.5}{s+4} + \frac{4}{s+3}$$

$$= \left( \frac{1}{2} - 4.5e^{-4t} + 4e^{-3t} \right) v(t).$$

Note:  $V_C^{step}(t) = 0$  (as expected)

$V_C^{step}(0) = \frac{1}{2}$  (from circuit)

$v(0^+) = 6V$  (from circuit, impulse response at  $t=0^+ \rightarrow V_C(0^+) = 6$ )

$$\rightarrow \left[ \cancel{\frac{dV_C^{step}}{dt}} \Big|_{t=0^+} \right] = 18 - 12 = 6V \quad (\text{matching also})$$